 


ECE 150 Digital Logic Design, Fall 2024  
**Project 1: 2-bit Arithmetic Logic Unit**  
Due October 9th 2024

Using any of the following ICs in JLab, *gates*, *muxes*, *demuxes*, *decoders*, implement a 2-bit Arithmetic Logic Unit (ALU) as a combinatorial logic circuit (no memory circuitry or sequential logic). Your ALU must accept two 2-bit words as input (A, B), a 4-bit op-code (Op) and output a single 2-bit word (Y).



Your ALU must be able to perform the following operations:

- (Op = 0000) No-op ( $Y = A$ )
- (Op = 0001) Binary Addition ( $Y = A + B$ )
- (Op = 0010) Binary Subtraction ( $Y = B - A$ , in two's complement)
- (Op = 0011) Logical Shift of A (ex. if  $A = 01$ , then  $Y = 1C_{in}$ )
- (Op = 0100) Bitwise OR ( $Y_n = A_n + B_n$ )
- (Op = 0101) Bitwise AND ( $Y_n = A_n B_n$ )
- (Op = 0110) Bitwise NOT ( $Y_n = \bar{A}_n$ )
- (Op = 0111) Bitwise XOR ( $Y_n = A_n \oplus B_n$ )

**You will demonstrate the correct output of your circuit at the beginning of class on the due-date, and submit a typed PDF report.**

**Circuit Requirements:**

- Provide inputs  $A_{1-0}$ ,  $B_{1-0}$ , and  $Op_{3-0}$  via three 4-input DIP switches (active-high) from left to right.
- Use no more than three breadboards.
- Use red wire for 5V and black for ground.
- Display your outputs on LEDs.

**Report Requirements:**

- Introduction: restate the problem in your own words
- Methods: detail how you arrived at your implementation. You must include,
  - truth-table(s)
  - a derivation of your final implemented expressions (boolean algebra or K-map)
  - logic diagram(s)
- Implementation: detail your circuit, including,
  - a picture of your circuit with labeled ICs and labeled subcircuits.
- Conclusion:
  - What are the pros and cons of your design?

## Grading:

- Correct circuit operation (demo) (45 pts)
- Report (45 pts)
- Scalable ALU (see additional circuit considerations below) (10 pts)

## Additional Considerations:

- Circuit
  - **Scalable ALU:** Can you combine ALUs with a classmate to create an 4-bit ALU? An 8-bit ALU? (+5 pts to project if 4-bit ALU demo'd, +5pts to project if 2N-bit ALU described in report)
  - Neatness (color coding, right-angles only, no crossing wires) (+2/100 pts to midterm exam)
  - Number of ICs used (+3/+1 points to midterm for fewest chips used, ranked by class).
- Report
  - Consistent typesetting
  - Schematics and diagrams done in CAD (or hand-drawn EXTREMELY NEATLY)
  - Correct use of technical terms
  - All Figures, Images, and Tables have captions and are referenced in the text

You may find it helpful to make use of simulation software, such as Logisim or Logisim-Evolution.